

# Ingredients for Perfect RF Transceiver

D. Teytelman

Dimtel, Inc., San Jose, CA, USA

November 4, 2015



# Outline

## 1 Introduction

## 2 Measurements and Surprises

- Single Tone ADC Characterization
- Spurs
- Amplifier Phase Noise
- Input Channel Coupling
- Output to Input Coupling
- Reflections



# Focus of this Tutorial

- I will focus on a fairly common modern approach to building LLRF:
  - ▶ Heterodyne downconverters for input
  - ▶ Digital signal processor with ADCs, FPGAs, and DACs
  - ▶ Heterodyne upconverters at the output
- Several advantages of converting to intermediate frequency (IF) instead of DC:
  - ▶ Single downconverter and ADC per channel;
  - ▶ Insensitive to DC offsets and drifts.
- Why not direct sampling?
  - ▶ Downconversion translates phase at RF directly to phase at IF, producing  $f_{RF}/f_{IF}$  improvement in ADC clock jitter sensitivity.



# Focus of this Tutorial

- I will focus on a fairly common modern approach to building LLRF:
  - ▶ Heterodyne downconverters for input
  - ▶ Digital signal processor with ADCs, FPGAs, and DACs
  - ▶ Heterodyne upconverters at the output
- Several advantages of converting to intermediate frequency (IF) instead of DC:
  - ▶ Single downconverter and ADC per channel;
  - ▶ Insensitive to DC offsets and drifts.
- Why not direct sampling?
  - ▶ Downconversion translates phase at RF directly to phase at IF, producing  $f_{RF}/f_{IF}$  improvement in ADC clock jitter sensitivity.




# Focus of this Tutorial

- I will focus on a fairly common modern approach to building LLRF:
  - ▶ Heterodyne downconverters for input
  - ▶ Digital signal processor with ADCs, FPGAs, and DACs
  - ▶ Heterodyne upconverters at the output
- Several advantages of converting to intermediate frequency (IF) instead of DC:
  - ▶ Single downconverter and ADC per channel;
  - ▶ Insensitive to DC offsets and drifts.
- Why not direct sampling?
  - ▶ Downconversion translates phase at RF directly to phase at IF, producing  $f_{RF}/f_{IF}$  improvement in ADC clock jitter sensitivity.



# Generic Receiver Block Diagram

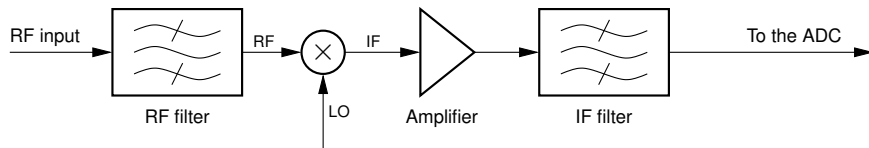


Local oscillator

- RF filter is optional;
- As is IF amplifier.
- At the IF port of the mixer both desired signal (lower sideband) at  $\omega_{\text{IF}} - \omega_{\text{LO}}$  and unwanted upper sideband at  $\omega_{\text{IF}} + \omega_{\text{LO}}$  are present;
- For the mixer to perform well, both upper and lower sidebands must be well terminated.




# Generic Receiver Block Diagram

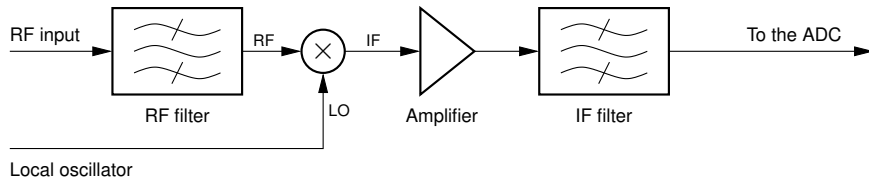

- RF filter is optional;
- As is IF amplifier.
- At the IF port of the mixer both desired signal (lower sideband) at  $\omega_{\text{rf}} - \omega_{\text{lo}}$  and unwanted upper sideband at  $\omega_{\text{rf}} + \omega_{\text{lo}}$  are present;
- For the mixer to perform well, both upper and lower sidebands must be well terminated.



# Generic Receiver Block Diagram

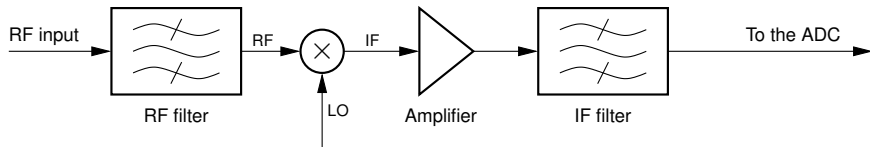


Local oscillator

- RF filter is optional;
- As is IF amplifier.
- At the IF port of the mixer both desired signal (lower sideband) at  $\omega_{\text{rf}} - \omega_{\text{lo}}$  and unwanted upper sideband at  $\omega_{\text{rf}} + \omega_{\text{lo}}$  are present;
- For the mixer to perform well, both upper and lower sidebands must be well terminated.





# Generic Receiver Block Diagram

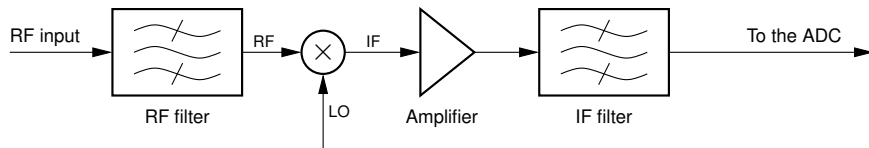


Local oscillator

- RF filter is optional;
- As is IF amplifier.
- At the IF port of the mixer both desired signal (lower sideband) at  $\omega_{rf} - \omega_{lo}$  and unwanted upper sideband at  $\omega_{rf} + \omega_{lo}$  are present;
- For the mixer to perform well, both upper and lower sidebands must be well terminated.



# Generic Receiver Block Diagram

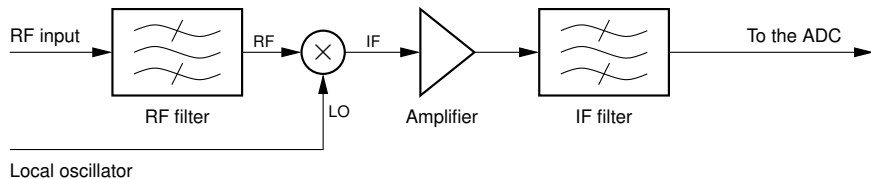

- RF filter is optional;
- As is IF amplifier.
- At the IF port of the mixer both desired signal (lower sideband) at  $\omega_{\text{rf}} - \omega_{\text{lo}}$  and unwanted upper sideband at  $\omega_{\text{rf}} + \omega_{\text{lo}}$  are present;
- For the mixer to perform well, both upper and lower sidebands must be well terminated.



# Main Difficulty in LLRF Receivers

- The secret to building low noise receivers is well known.
- Friis equation for the noise factor:  $F = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots$
- Use a high gain low noise amplifier as the very first stage of your signal chain.
- Cascade noise figure is then dominated by the first stage, greatly relaxing the requirements for the rest of the chain.
- Unfortunately this approach assumes we start with very low amplitude signals;
- In LLRF we typically start with very large signals, so the first stage is often a 20–30 dB attenuator.



# Main Difficulty in LLRF Receivers

- The secret to building low noise receivers is well known.
- Friis equation for the noise factor:  $F = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots$
- Use a high gain low noise amplifier as the very first stage of your signal chain.
- Cascade noise figure is then dominated by the first stage, greatly relaxing the requirements for the rest of the chain.
- Unfortunately this approach assumes we start with very low amplitude signals;
- In LLRF we typically start with very large signals, so the first stage is often a 20–30 dB attenuator.




# Main Difficulty in LLRF Receivers

- The secret to building low noise receivers is well known.
- Friis equation for the noise factor:  $F = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots$
- Use a high gain low noise amplifier as the very first stage of your signal chain.
- Cascade noise figure is then dominated by the first stage, greatly relaxing the requirements for the rest of the chain.
- Unfortunately this approach assumes we start with very low amplitude signals;
- In LLRF we typically start with very large signals, so the first stage is often a 20–30 dB attenuator.



# Receiver Block Diagram

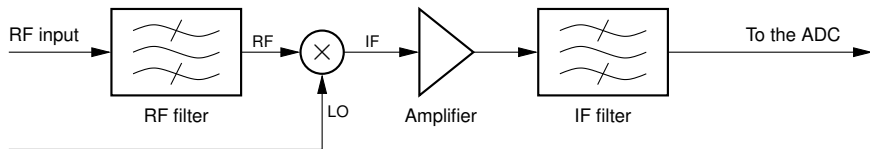


Local oscillator

- To maintain linearity, RF port of the mixer has to stay 10–20 dB below the LO port;
- With 13 dBm mixers, you can't get much above 0 dBm without introducing significant distortion;
- 8 channel module with 13 dBm LO needs 27 dBm (0.5W) input;
- Going to 17, 23, or 27 dBm gets impractical very quickly;
- Mixer output is typically too small for the ADCs, some voltage gain is needed.




# Receiver Block Diagram

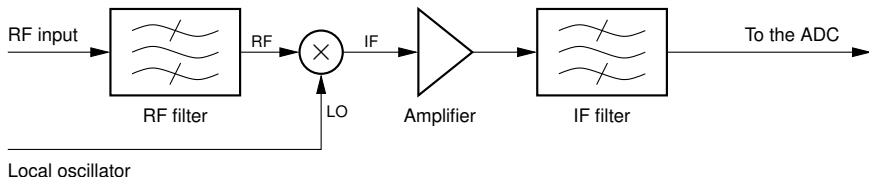

- To maintain linearity, RF port of the mixer has to stay 10–20 dB below the LO port;
- With 13 dBm mixers, you can't get much above 0 dBm without introducing significant distortion;
- 8 channel module with 13 dBm LO needs 27 dBm (0.5W) input;
- Going to 17, 23, or 27 dBm gets impractical very quickly;
- Mixer output is typically too small for the ADCs, some voltage gain is needed.



# Receiver Block Diagram

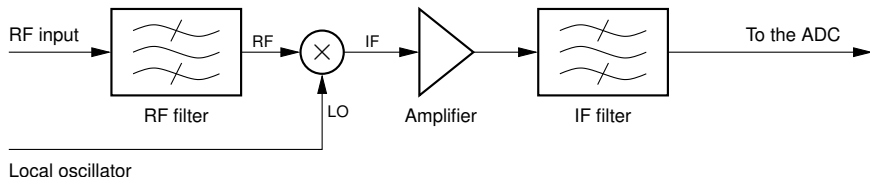


- To maintain linearity, RF port of the mixer has to stay 10–20 dB below the LO port;
- With 13 dBm mixers, you can't get much above 0 dBm without introducing significant distortion;
- 8 channel module with 13 dBm LO needs 27 dBm (0.5W) input;
- Going to 17, 23, or 27 dBm gets impractical very quickly;
- Mixer output is typically too small for the ADCs, some voltage gain is needed.






# Receiver Block Diagram

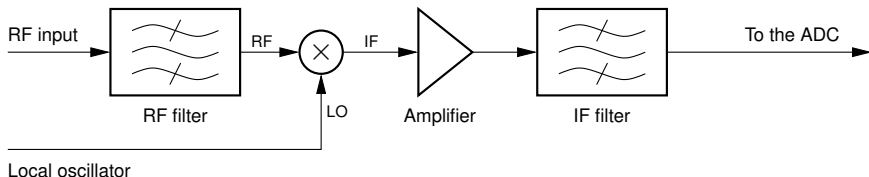

- To maintain linearity, RF port of the mixer has to stay 10–20 dB below the LO port;
- With 13 dBm mixers, you can't get much above 0 dBm without introducing significant distortion;
- 8 channel module with 13 dBm LO needs 27 dBm (0.5W) input;
- Going to 17, 23, or 27 dBm gets impractical very quickly;
- Mixer output is typically too small for the ADCs, some voltage gain is needed.




# Receiver Block Diagram

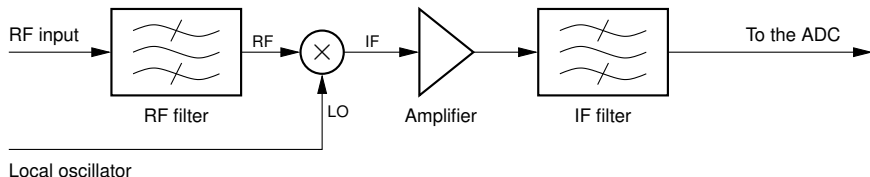

- To maintain linearity, RF port of the mixer has to stay 10–20 dB below the LO port;
- With 13 dBm mixers, you can't get much above 0 dBm without introducing significant distortion;
- 8 channel module with 13 dBm LO needs 27 dBm (0.5W) input;
- Going to 17, 23, or 27 dBm gets impractical very quickly;
- Mixer output is typically too small for the ADCs, some voltage gain is needed.



# Receiver Block Diagram

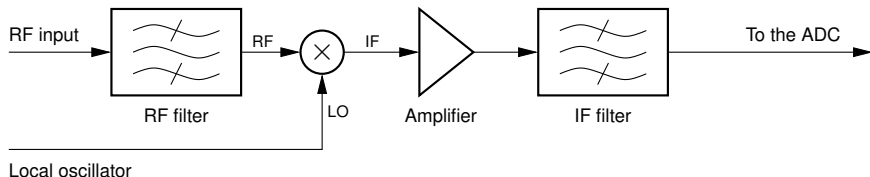

- To maintain linearity, RF port of the mixer has to stay 10–20 dB below the LO port;
- With 13 dBm mixers, you can't get much above 0 dBm without introducing significant distortion;
- 8 channel module with 13 dBm LO needs 27 dBm (0.5W) input;
- Going to 17, 23, or 27 dBm gets impractical very quickly;
- Mixer output is typically too small for the ADCs, some voltage gain is needed.



# Enemies of the Perfect Transceiver

- Channel to channel coupling;
- Spurious signals;
- Gain and phase drifts;
- Phase noise;
- Broadband noise;
- Distortion.



# Outline

## 1 Introduction

## 2 Measurements and Surprises

- Single Tone ADC Characterization
- Spurs
- Amplifier Phase Noise
- Input Channel Coupling
- Output to Input Coupling
- Reflections



# In This Section

- Learning from your mistakes is a good way to learn;
- But learning from the mistakes of others is even better;
- I will present here a mix of measurement techniques for quantifying transceiver performance;
- Many of these measurements have lead to discoveries of unwanted behavior;
- I'll try to explain the mechanisms and to offer solutions.



# In This Section

- Learning from your mistakes is a good way to learn;
- But learning from the mistakes of others is even better;
- I will present here a mix of measurement techniques for quantifying transceiver performance;
- Many of these measurements have lead to discoveries of unwanted behavior;
- I'll try to explain the mechanisms and to offer solutions.



# In This Section

- Learning from your mistakes is a good way to learn;
- But learning from the mistakes of others is even better;
- I will present here a mix of measurement techniques for quantifying transceiver performance;
- Many of these measurements have lead to discoveries of unwanted behavior;
- I'll try to explain the mechanisms and to offer solutions.





# In This Section

- Learning from your mistakes is a good way to learn;
- But learning from the mistakes of others is even better;
- I will present here a mix of measurement techniques for quantifying transceiver performance;
- Many of these measurements have lead to discoveries of unwanted behavior;
- I'll try to explain the mechanisms and to offer solutions.



# In This Section

- Learning from your mistakes is a good way to learn;
- But learning from the mistakes of others is even better;
- I will present here a mix of measurement techniques for quantifying transceiver performance;
- Many of these measurements have lead to discoveries of unwanted behavior;
- I'll try to explain the mechanisms and to offer solutions.



# Outline


## 1 Introduction

## 2 Measurements and Surprises

- Single Tone ADC Characterization
  - Spurs
  - Amplifier Phase Noise
  - Input Channel Coupling
  - Output to Input Coupling
  - Reflections




# Basic Measurement

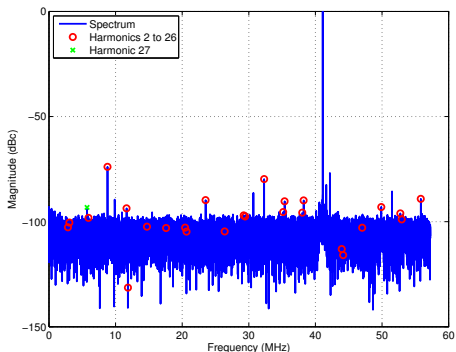

- Set input signal to CW frequency in an exact FFT bin;
- Capture 16–64k samples;
- Standard calculation to extract SNR, SINAD, ENOB, SFDR;
- Hardware check - identify stuck or shorted ADC bits.
- Rich harmonic content;
- Reference channel coupling at 41.7 MHz and an intermodulation line.




# Basic Measurement

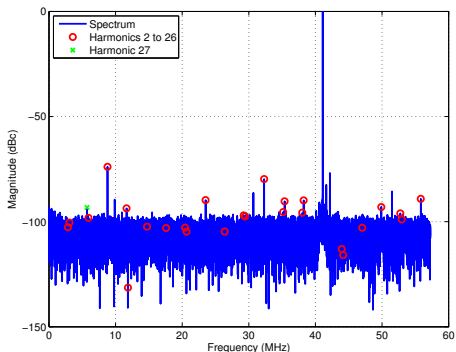

- Set input signal to CW frequency in an exact FFT bin;
- Capture 16–64k samples;
- Standard calculation to extract SNR, SINAD, ENOB, SFDR;
- Hardware check - identify stuck or shorted ADC bits.
- Rich harmonic content;
- Reference channel coupling at 41.7 MHz and an intermodulation line.




# Basic Measurement

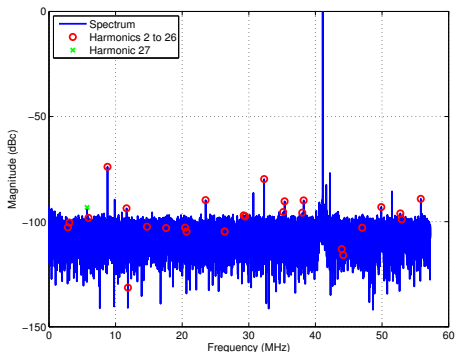

- Set input signal to CW frequency in an exact FFT bin;
- Capture 16–64k samples;
- Standard calculation to extract SNR, SINAD, ENOB, SFDR;
- Hardware check - identify stuck or shorted ADC bits.
- Rich harmonic content;
- Reference channel coupling at 41.7 MHz and an intermodulation line.




# Basic Measurement

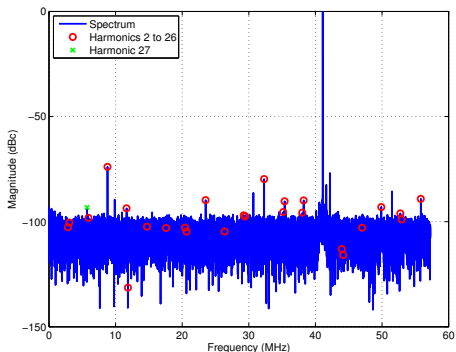

- Set input signal to CW frequency in an exact FFT bin;
- Capture 16–64k samples;
- Standard calculation to extract SNR, SINAD, ENOB, SFDR;
- Hardware check - identify stuck or shorted ADC bits.
- Rich harmonic content;
- Reference channel coupling at 41.7 MHz and an intermodulation line.



# Basic Measurement

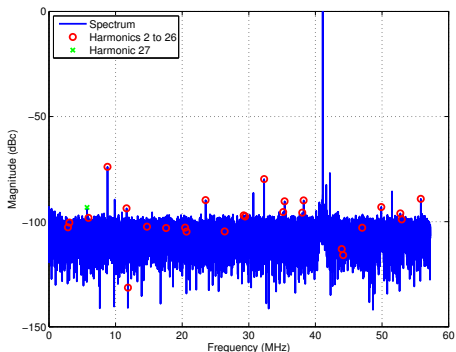


- Set input signal to CW frequency in an exact FFT bin;
- Capture 16–64k samples;
- Standard calculation to extract SNR, SINAD, ENOB, SFDR;
- Hardware check - identify stuck or shorted ADC bits.
- Rich harmonic content;
- Reference channel coupling at 41.7 MHz and an intermodulation line.






# Basic Measurement

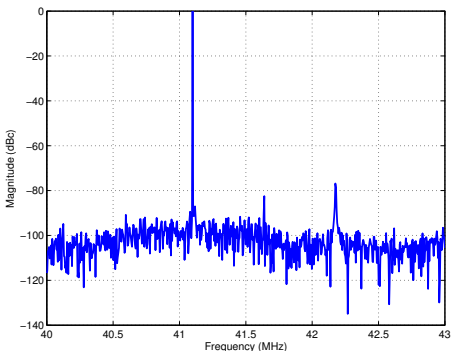

- Set input signal to CW frequency in an exact FFT bin;
- Capture 16–64k samples;
- Standard calculation to extract SNR, SINAD, ENOB, SFDR;
- Hardware check - identify stuck or shorted ADC bits.
- Rich harmonic content;
- Reference channel coupling at 41.7 MHz and an intermodulation line.




# Avoiding FFT Windowing

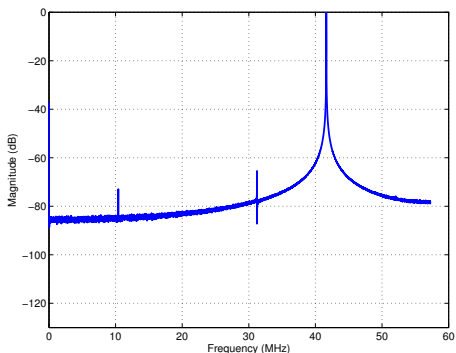

- Capture 24576 samples of CW IF signal;
- IF to sampling ratio 4/11;
- A lot of spectral leakage;
- Standard approach is to window time-domain signal (Blackman);
- Another way is to trim the data record to leave an integer number of periods ( $24574 = 2234 * 11$ ).




# Avoiding FFT Windowing

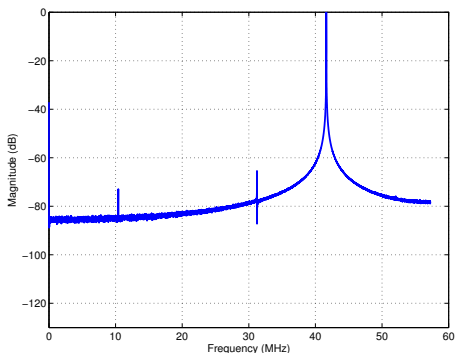

- Capture 24576 samples of CW IF signal;
- IF to sampling ratio 4/11;
- A lot of spectral leakage;
- Standard approach is to window time-domain signal (Blackman);
- Another way is to trim the data record to leave an integer number of periods ( $24574 = 2234 * 11$ ).




# Avoiding FFT Windowing

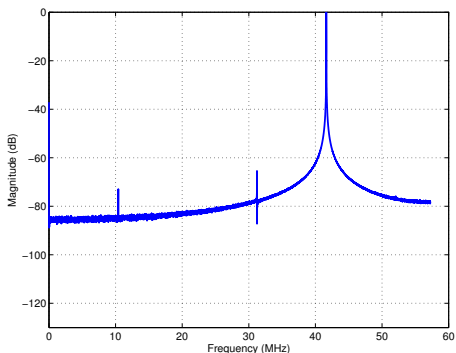

- Capture 24576 samples of CW IF signal;
- IF to sampling ratio 4/11;
- A lot of spectral leakage;
- Standard approach is to window time-domain signal (Blackman);
- Another way is to trim the data record to leave an integer number of periods ( $24574 = 2234 * 11$ ).




# Avoiding FFT Windowing

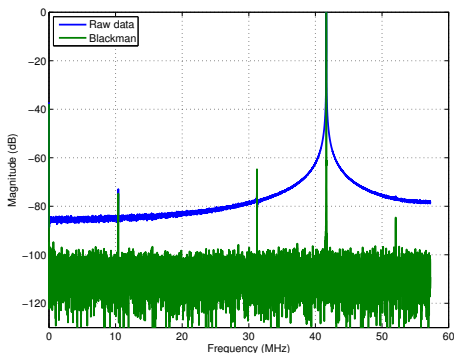

- Capture 24576 samples of CW IF signal;
- IF to sampling ratio 4/11;
- A lot of spectral leakage;
- Standard approach is to window time-domain signal (Blackman);
- Another way is to trim the data record to leave an integer number of periods ( $24574 = 2234 * 11$ ).




# Avoiding FFT Windowing

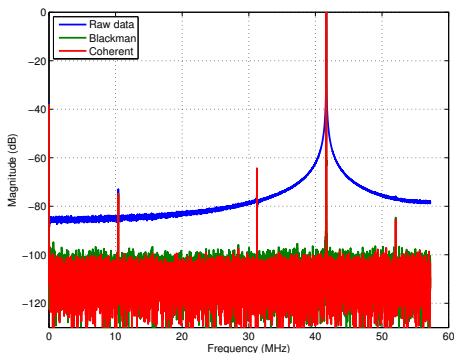

- Capture 24576 samples of CW IF signal;
- IF to sampling ratio 4/11;
- A lot of spectral leakage;
- Standard approach is to window time-domain signal (Blackman);
- Another way is to trim the data record to leave an integer number of periods ( $24574 = 2234 * 11$ ).




# Avoiding FFT Windowing, Continued

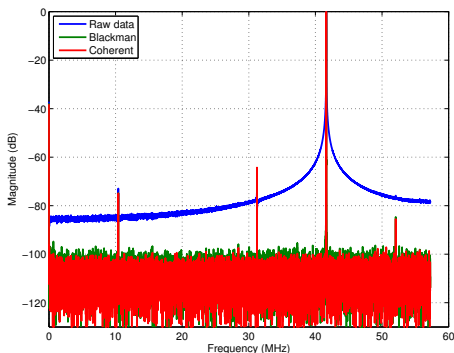

- This is called coherent sampling;
- Not much difference between windowed spectrum and coherent sampling one;
- What if we zoom in?
- Log scale vs. offset frequency;
- Coherent sampling gives us a way to measure noise density within one FFT bin of the carrier!



# Avoiding FFT Windowing, Continued

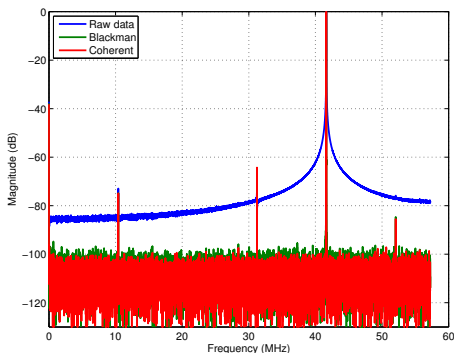


- This is called coherent sampling;
- Not much difference between windowed spectrum and coherent sampling one;
- What if we zoom in?
- Log scale vs. offset frequency;
- Coherent sampling gives us a way to measure noise density within one FFT bin of the carrier!






# Avoiding FFT Windowing, Continued

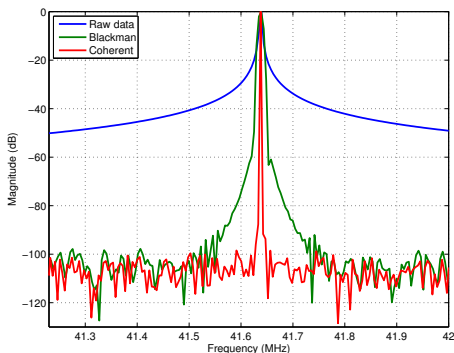

- This is called coherent sampling;
- Not much difference between windowed spectrum and coherent sampling one;
- What if we zoom in?
  - Log scale vs. offset frequency;
  - Coherent sampling gives us a way to measure noise density within one FFT bin of the carrier!




# Avoiding FFT Windowing, Continued

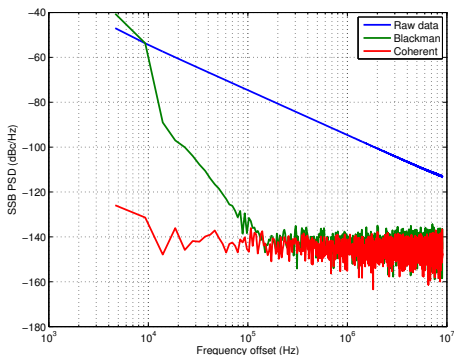

- This is called coherent sampling;
- Not much difference between windowed spectrum and coherent sampling one;
- What if we zoom in?
- Log scale vs. offset frequency;
- Coherent sampling gives us a way to measure noise density within one FFT bin of the carrier!




# Avoiding FFT Windowing, Continued

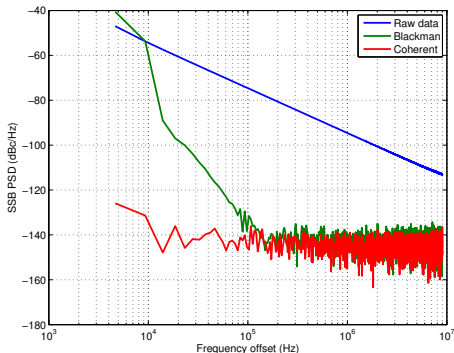

- This is called coherent sampling;
- Not much difference between windowed spectrum and coherent sampling one;
- What if we zoom in?
- Log scale vs. offset frequency;
- Coherent sampling gives us a way to measure noise density within one FFT bin of the carrier!




# SSB Noise Density

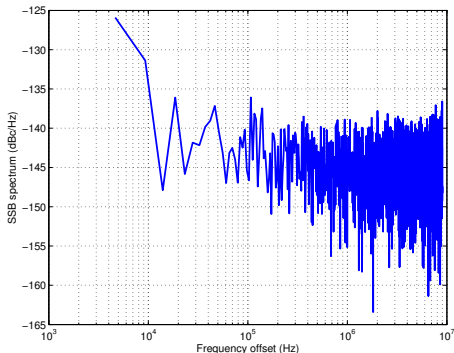

- FFT of a single acquisition;
- An average of 1000 acquisitions;
- Use two channels, average of 1000 cross-correlated acquisitions;
- Uncorrelated noise sources are averaged out
  - ▶ Averaged out: channel thermal noise, ADC quantization and aperture jitter;
  - ▶ Remain: source noise, common LO and clock noise.




# SSB Noise Density

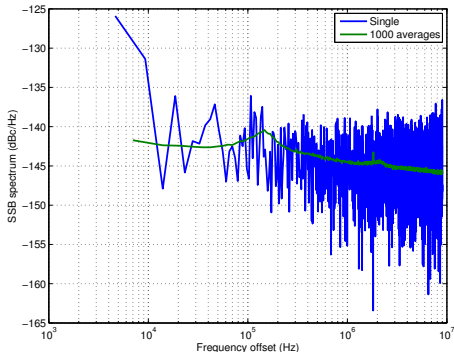

- FFT of a single acquisition;
- An average of 1000 acquisitions;
- Use two channels, average of 1000 cross-correlated acquisitions;
- Uncorrelated noise sources are averaged out
  - ▶ Averaged out: channel thermal noise, ADC quantization and aperture jitter;
  - ▶ Remain: source noise, common LO and clock noise.




# SSB Noise Density

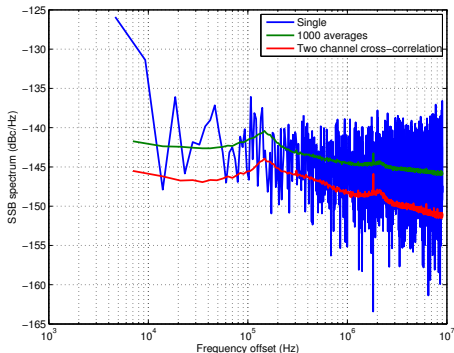

- FFT of a single acquisition;
- An average of 1000 acquisitions;
- Use two channels, average of 1000 cross-correlated acquisitions;
- Uncorrelated noise sources are averaged out
  - ▶ Averaged out: channel thermal noise, ADC quantization and aperture jitter;
  - ▶ Remain: source noise, common LO and clock noise.



# SSB Noise Density

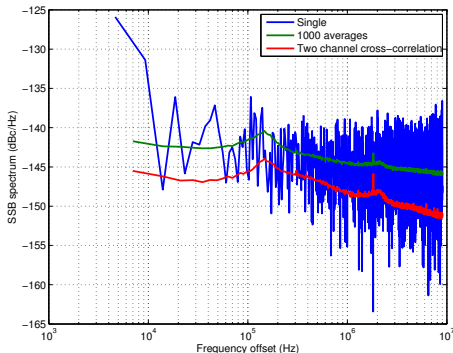

- FFT of a single acquisition;
- An average of 1000 acquisitions;
- Use two channels, average of 1000 cross-correlated acquisitions;
- Uncorrelated noise sources are averaged out
  - ▶ Averaged out: channel thermal noise, ADC quantization and aperture jitter;
  - ▶ Remain: source noise, common LO and clock noise.



# Outline

## 1 Introduction


## 2 Measurements and Surprises

- Single Tone ADC Characterization
- **Spurs**
- Amplifier Phase Noise
- Input Channel Coupling
- Output to Input Coupling
- Reflections






# Hunting Spurs

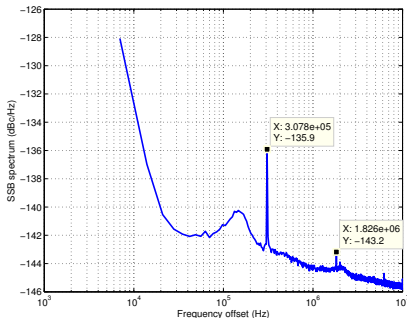

- Single channel spectrum, 308 kHz spur;
- Comes from DC-DC converter driving LO generator bulk supply;
- Between DC-DC converter and RF supplies:
  - ▶ An RC filter;
  - ▶ Low-noise LDO regulator;
  - ▶ Tens of bypass capacitors.
- Lower ESR RC filter, 2.2 dB improvement;
- 10 2.2  $\mu$ F LDO input capacitors replaced with 22  $\mu$ F.




# Hunting Spurs

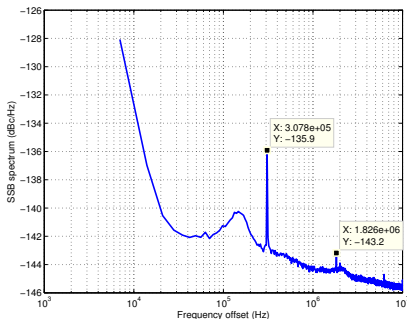

- Single channel spectrum, 308 kHz spur;
- Comes from DC-DC converter driving LO generator bulk supply;
- Between DC-DC converter and RF supplies:
  - ▶ An RC filter;
  - ▶ Low-noise LDO regulator;
  - ▶ Tens of bypass capacitors.
- Lower ESR RC filter, 2.2 dB improvement;
- 10 2.2  $\mu$ F LDO input capacitors replaced with 22  $\mu$ F.




# Hunting Spurs

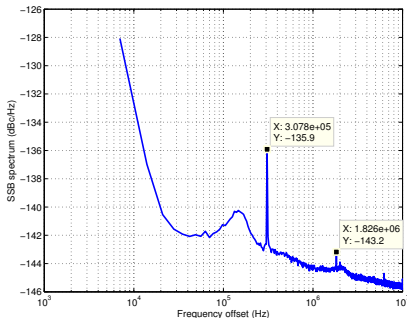

- Single channel spectrum, 308 kHz spur;
- Comes from DC-DC converter driving LO generator bulk supply;
- Between DC-DC converter and RF supplies:
  - ▶ An RC filter;
  - ▶ Low-noise LDO regulator;
  - ▶ Tens of bypass capacitors.
- Lower ESR RC filter, 2.2 dB improvement;
- 10 2.2  $\mu$ F LDO input capacitors replaced with 22  $\mu$ F.




# Hunting Spurs

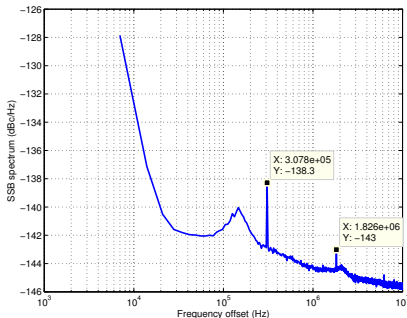

- Single channel spectrum, 308 kHz spur;
- Comes from DC-DC converter driving LO generator bulk supply;
- Between DC-DC converter and RF supplies:
  - ▶ An RC filter;
  - ▶ Low-noise LDO regulator;
  - ▶ Tens of bypass capacitors.
- Lower ESR RC filter, 2.2 dB improvement;
- 10  $2.2 \mu\text{F}$  LDO input capacitors replaced with  $22 \mu\text{F}$ .



# Hunting Spurs

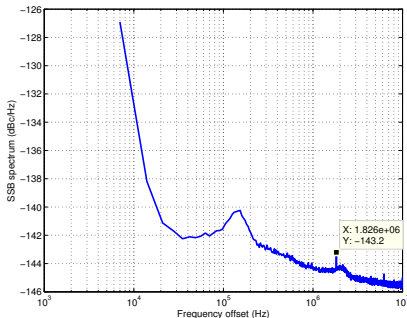


- Single channel spectrum, 308 kHz spur;
- Comes from DC-DC converter driving LO generator bulk supply;
- Between DC-DC converter and RF supplies:
  - ▶ An RC filter;
  - ▶ Low-noise LDO regulator;
  - ▶ Tens of bypass capacitors.
- Lower ESR RC filter, 2.2 dB improvement;
- 10  $2.2 \mu\text{F}$  LDO input capacitors replaced with  $22 \mu\text{F}$ .



# Hunting Spurs

## RIPPLE REJECTION vs FREQUENCY

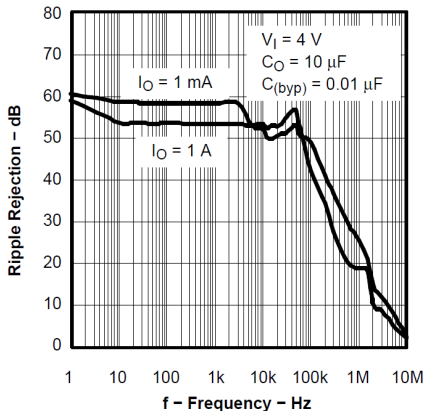


- From TI TPS796XX datasheet;
- LDO might have 60 dB power supply rejection at low frequencies;
- But at 300 kHz you are lucky if you get 30 dB PSRR;
- Turns out a ferrite on the power lines between supply and the LO board works wonders;
- 2-3  $\Omega$  impedance at 300 kHz is all it takes.



# Hunting Spurs

## RIPPLE REJECTION vs FREQUENCY

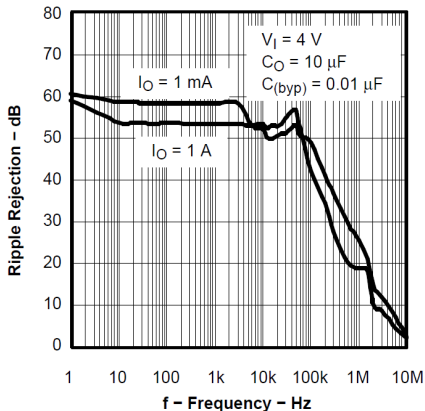


- From TI TPS796XX datasheet;
- LDO might have 60 dB power supply rejection at low frequencies;
- But at 300 kHz you are lucky if you get 30 dB PSRR;
- Turns out a ferrite on the power lines between supply and the LO board works wonders;
- 2-3  $\Omega$  impedance at 300 kHz is all it takes.



# Hunting Spurs

## RIPPLE REJECTION VS FREQUENCY

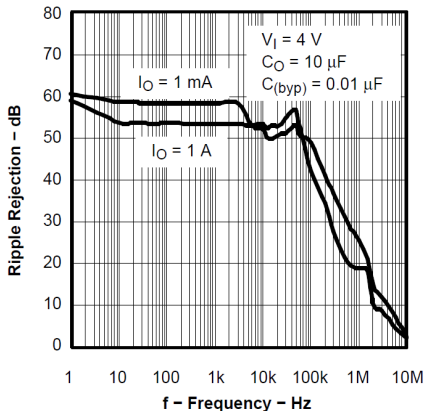


- From TI TPS796XX datasheet;
- LDO might have 60 dB power supply rejection at low frequencies;
- But at 300 kHz you are lucky if you get 30 dB PSRR;
- Turns out a ferrite on the power lines between supply and the LO board works wonders;
- 2-3  $\Omega$  impedance at 300 kHz is all it takes.





# Hunting Spurs

## RIPPLE REJECTION VS FREQUENCY

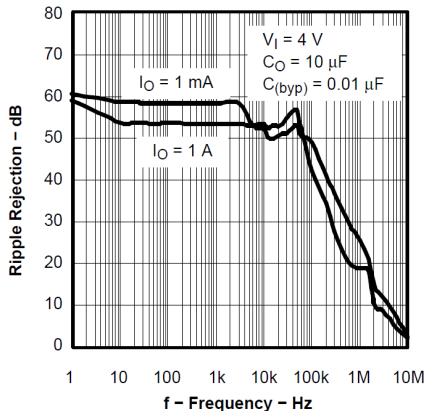

- From TI TPS796XX datasheet;
- LDO might have 60 dB power supply rejection at low frequencies;
- But at 300 kHz you are lucky if you get 30 dB PSRR;
- Turns out a ferrite on the power lines between supply and the LO board works wonders;
- 2-3  $\Omega$  impedance at 300 kHz is all it takes.



# Outline


## 1 Introduction

## 2 Measurements and Surprises

- Single Tone ADC Characterization
- Spurs
- **Amplifier Phase Noise**
- Input Channel Coupling
- Output to Input Coupling
- Reflections




# Measuring Additive Phase Noise

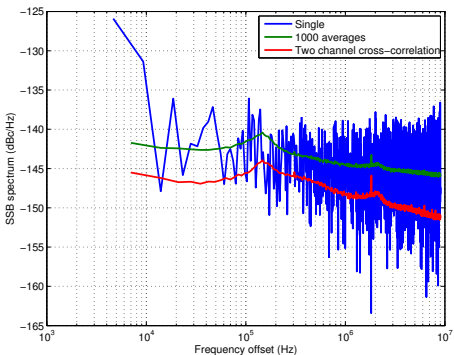

- This is not a demodulated signal, so both amplitude and phase noise are included;
- Comparison with demodulated phase noise measurements on the same system shows that phase noise dominates below 100 kHz;
- Use the setup to investigate additive phase noise contribution of amplifiers.




# Measuring Additive Phase Noise

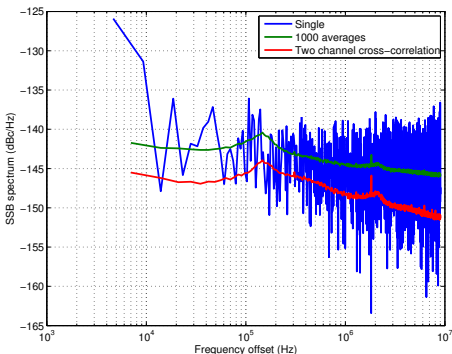

- This is not a demodulated signal, so both amplitude and phase noise are included;
- Comparison with demodulated phase noise measurements on the same system shows that phase noise dominates below 100 kHz;
- Use the setup to investigate additive phase noise contribution of amplifiers.



# Measuring Additive Phase Noise

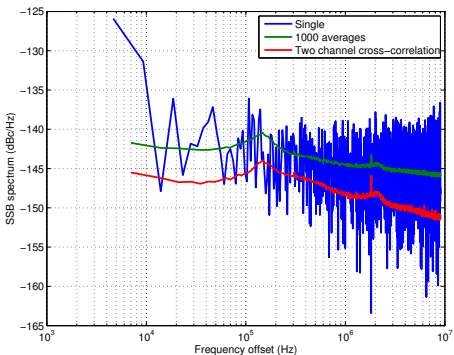

- This is not a demodulated signal, so both amplitude and phase noise are included;
- Comparison with demodulated phase noise measurements on the same system shows that phase noise dominates below 100 kHz;
- Use the setup to investigate additive phase noise contribution of amplifiers.



# Two Amplifiers

## Measured Parameters

Device	Gain (dB)	NF (dB)
MGA-31589	19.9	1.15
SKY65162	23.5	4.45

- Two amplifiers (LO drive candidates);
- Phase noise is dramatically different between the two;




# Two Amplifiers

## Measured Parameters

Device	Gain (dB)	NF (dB)
MGA-31589	19.9	1.15
SKY65162	23.5	4.45

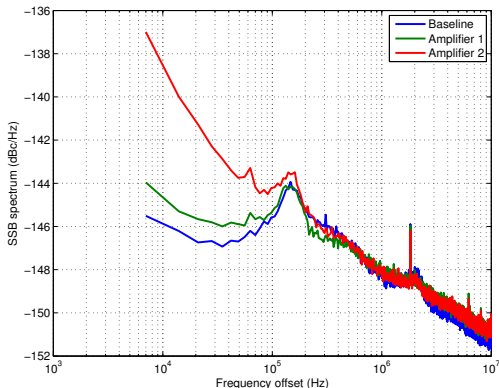
- Two amplifiers (LO drive candidates);
- Phase noise is dramatically different between the two;



# Two Amplifiers

## Measured Parameters

Device	Gain (dB)	NF (dB)
MGA-31589	19.9	1.15
SKY65162	23.5	4.45

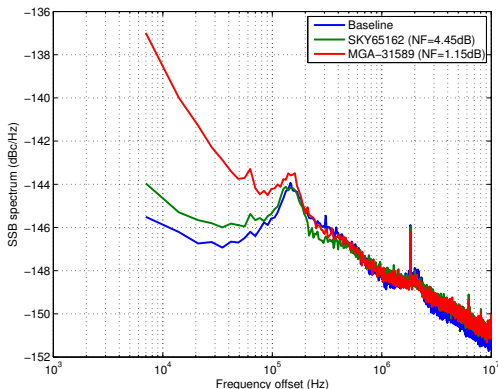

- Two amplifiers (LO drive candidates);
- Phase noise is dramatically different between the two;
- Wideband noise figure tells you little about the phase noise performance;
- Manufacturers rarely (never) talk about phase noise performance.





# Outline

## 1 Introduction

## 2 Measurements and Surprises

- Single Tone ADC Characterization
- Spurs
- Amplifier Phase Noise
- **Input Channel Coupling**
- Output to Input Coupling
- Reflections



# Channel to Channel Coupling: Measurements

## Standalone board

0	-77	-90	-101
-69	0	-75	-90
-79	-76	0	-70
-89	-89	-83	0

## Cold plate, thermal gap filler

0	-61	-61	-63
-58	0	-60	-64
-61	-61	0	-63
-65	-63	-64	0

- A typical coupling matrix for four channels (dB);
- The same board is mounted 1.27 mm above the cold plate;
- A different gap filler magically fixes the problem.



# Channel to Channel Coupling: Measurements

## Standalone board

0	-77	-90	-101
-69	0	-75	-90
-79	-76	0	-70
-89	-89	-83	0

## Cold plate, thermal gap filler

0	-61	-61	-63
-58	0	-60	-64
-61	-61	0	-63
-65	-63	-64	0

- A typical coupling matrix for four channels (dB);
- The same board is mounted 1.27 mm above the cold plate;
- A different gap filler magically fixes the problem.



# Channel to Channel Coupling: Measurements

## Standalone board

0	-77	-90	-101
-69	0	-75	-90
-79	-76	0	-70
-89	-89	-83	0


## A different thermal gap filler

0	-77	-88	-91
-68	0	-74	-88
-77	-75	0	-70
-89	-86	-81	0

- A typical coupling matrix for four channels (dB);
- The same board is mounted 1.27 mm above the cold plate;
- A different gap filler magically fixes the problem.



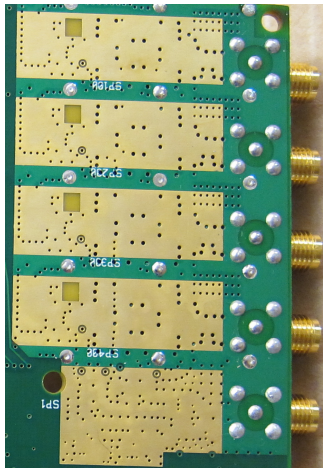
# Channel to Channel Coupling: Investigation



- What causes coupling and why do different materials behave differently?
- Increased coupling is due to the thermal gap filler in the area under four input SMA connectors.
- Dielectric constants:
  - ▶ Bergquist GP3000S30-0.060: 7@1 kHz
  - ▶ Laird Tflex 660 DC1: 3.31@1 MHz
- 2 mm center conductor pad, parasitic capacitance to the plate:
  - ▶ 0.65 pF
  - ▶ 0.3 pF
- Clearly there is more going on:  $\epsilon_r$  change with frequency, etc.



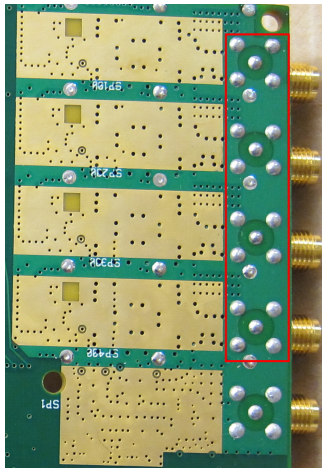
# Channel to Channel Coupling: Investigation



- What causes coupling and why do different materials behave differently?
- Increased coupling is due to the thermal gap filler in the area under four input SMA connectors.
- Dielectric constants:
  - ▶ Bergquist GP3000S30-0.060: 7@1 kHz
  - ▶ Laird Tflex 660 DC1: 3.31@1 MHz
- 2 mm center conductor pad, parasitic capacitance to the plate:
  - ▶ 0.65 pF
  - ▶ 0.3 pF
- Clearly there is more going on:  $\epsilon_r$  change with frequency, etc.



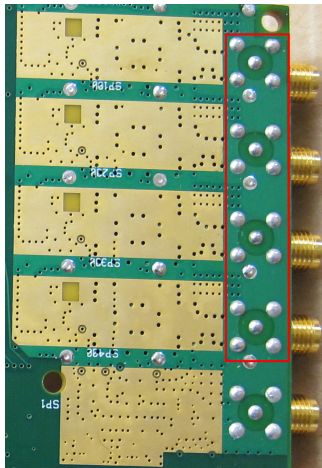
# Channel to Channel Coupling: Investigation



- What causes coupling and why do different materials behave differently?
- Increased coupling is due to the thermal gap filler in the area under four input SMA connectors.
- Dielectric constants:
  - ▶ Bergquist GP3000S30-0.060: 7@1 kHz
  - ▶ Laird Tflex 660 DC1: 3.31@1 MHz
- 2 mm center conductor pad, parasitic capacitance to the plate:
  - ▶ 0.65 pF
  - ▶ 0.3 pF
- Clearly there is more going on:  $\epsilon_r$  change with frequency, etc.


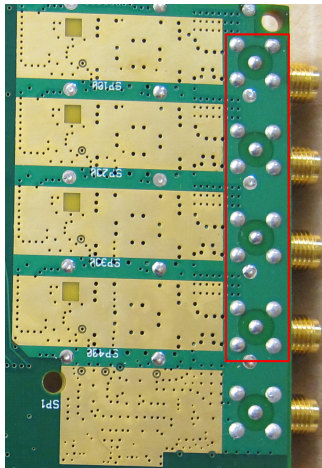
# Channel to Channel Coupling: Investigation




- What causes coupling and why do different materials behave differently?
- Increased coupling is due to the thermal gap filler in the area under four input SMA connectors.
- Dielectric constants:
  - ▶ Bergquist GP3000S30-0.060: 7@1 kHz
  - ▶ Laird Tflex 660 DC1: 3.31@1 MHz
- 2 mm center conductor pad, parasitic capacitance to the plate:
  - ▶ 0.65 pF
  - ▶ 0.3 pF
- Clearly there is more going on:  $\epsilon_r$  change with frequency, etc.




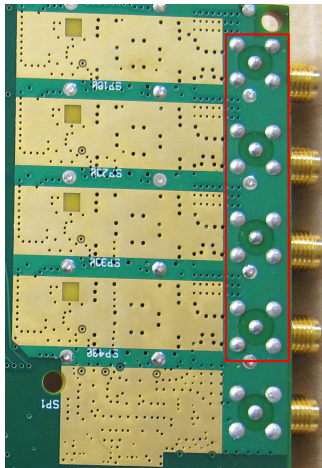
# Channel to Channel Coupling: Investigation



- What causes coupling and why do different materials behave differently?
- Increased coupling is due to the thermal gap filler in the area under four input SMA connectors.
- Dielectric constants:
  - ▶ Bergquist GP3000S30-0.060: 7@1 kHz
  - ▶ Laird Tflex 660 DC1: 3.31@1 MHz
- 2 mm center conductor pad, parasitic capacitance to the plate:
  - ▶ 0.65 pF
  - ▶ 0.3 pF
- Clearly there is more going on:  $\epsilon_r$  change with frequency, etc.



# Learning from Mistakes

- Important point: when we design our systems, we necessarily simplify things and make assumptions;
- However carefully you simulate your design, there are always features you leave out;
- There is no substitute for the physical test bench and methodical troubleshooting;
- With experience, you can avoid some (but not all) of these mistakes;
- Building small prototype boards that isolate a section of the design is a good way to break the problem into manageable pieces.



# Learning from Mistakes

- Important point: when we design our systems, we necessarily simplify things and make assumptions;
- However carefully you simulate your design, there are always features you leave out;
- There is no substitute for the physical test bench and methodical troubleshooting;
- With experience, you can avoid some (but not all) of these mistakes;
- Building small prototype boards that isolate a section of the design is a good way to break the problem into manageable pieces.



# Learning from Mistakes

- Important point: when we design our systems, we necessarily simplify things and make assumptions;
- However carefully you simulate your design, there are always features you leave out;
- There is no substitute for the physical test bench and methodical troubleshooting;
- With experience, you can avoid some (but not all) of these mistakes;
- Building small prototype boards that isolate a section of the design is a good way to break the problem into manageable pieces.



# Learning from Mistakes

- Important point: when we design our systems, we necessarily simplify things and make assumptions;
- However carefully you simulate your design, there are always features you leave out;
- There is no substitute for the physical test bench and methodical troubleshooting;
- With experience, you can avoid some (but not all) of these mistakes;
- Building small prototype boards that isolate a section of the design is a good way to break the problem into manageable pieces.



# Outline



## 1 Introduction

## 2 Measurements and Surprises

- Single Tone ADC Characterization
- Spurs
- Amplifier Phase Noise
- Input Channel Coupling
- **Output to Input Coupling**
- Reflections



# Example of Strong Coupling

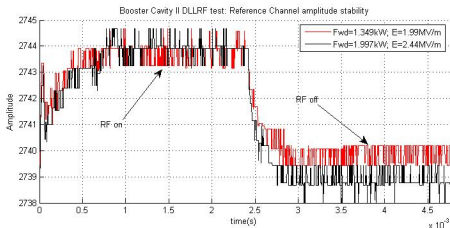
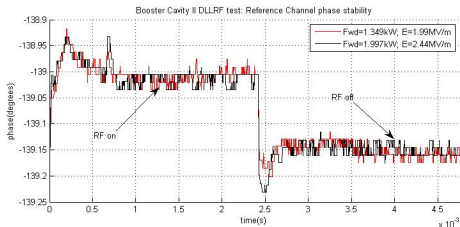


- Reference channel shifts during the output pulse;
- Change of 0.15%, 0.15°, -50 dB error vector;
- Coupling path — LO distribution:

- ▶ A 6-way splitter supplies LO to 4 input and 2 output channels;
- ▶ Isolation through the LO network is 23 dB at best;
- ▶ Coupling from output (drive) and from inputs (field, forward power).



# Example of Strong Coupling

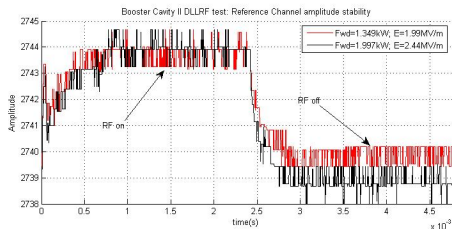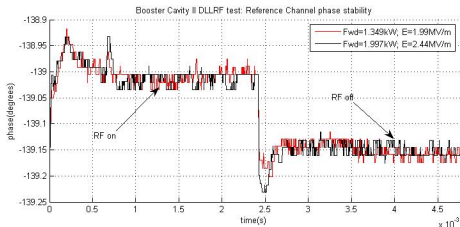



- Reference channel shifts during the output pulse;
- Change of 0.15%, 0.15°, -50 dB error vector;
- Coupling path — LO distribution:

- ▶ A 6-way splitter supplies LO to 4 input and 2 output channels;
- ▶ Isolation through the LO network is 23 dB at best;
- ▶ Coupling from output (drive) and from inputs (field, forward power).








# Example of Strong Coupling

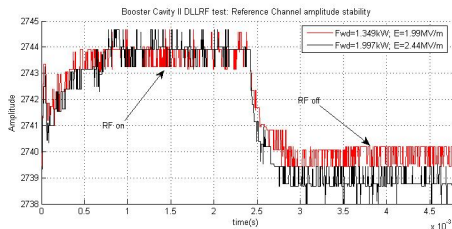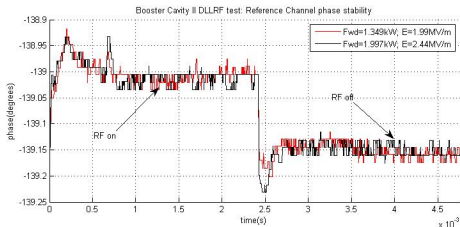

- Reference channel shifts during the output pulse;
- Change of 0.15%, 0.15°, -50 dB error vector;
- Coupling path — LO distribution:
  - ▶ A 6-way splitter supplies LO to 4 input and 2 output channels;
  - ▶ Isolation through the LO network is 23 dB at best;
  - ▶ Coupling from output (drive) and from inputs (field, forward power).






# A Cleaner Setup

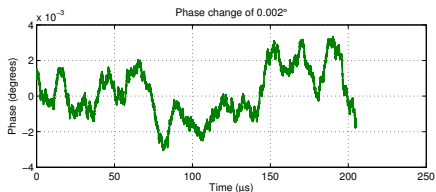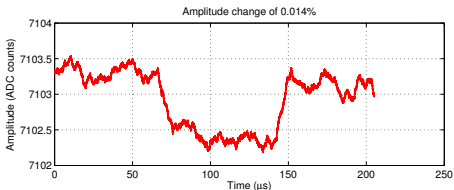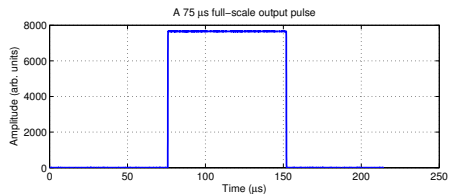

- 75  $\mu\text{s}$  output pulse (full scale);
- Isolation is around 77 dB;
- Connect the output to one of the inputs, still 74 dB;
- 8-way splitter: 3 stages of 90° hybrids;




# A Cleaner Setup

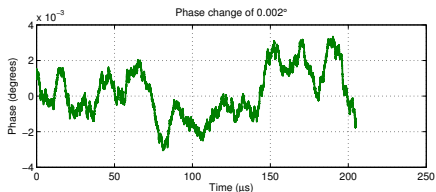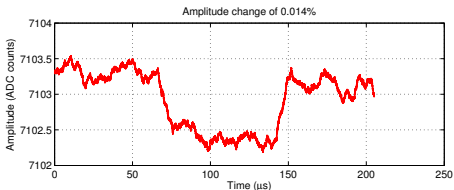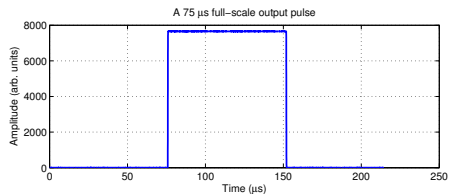

- 75  $\mu\text{s}$  output pulse (full scale);
- Isolation is around 77 dB;
- Connect the output to one of the inputs, still 74 dB;
- 8-way splitter: 3 stages of 90° hybrids;




# A Cleaner Setup

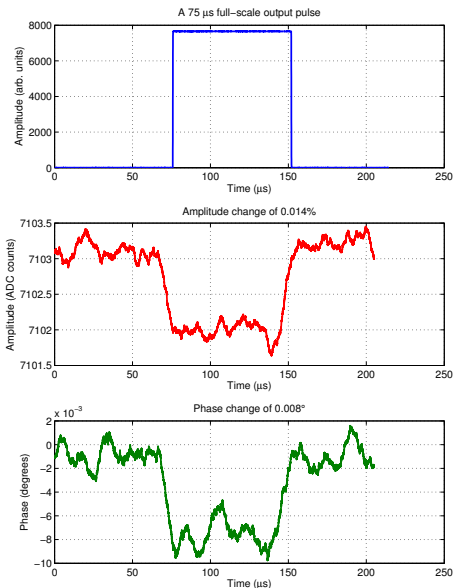

- 75  $\mu\text{s}$  output pulse (full scale);
- Isolation is around 77 dB;
- Connect the output to one of the inputs, still 74 dB;
- 8-way splitter: 3 stages of 90° hybrids;



# A Cleaner Setup

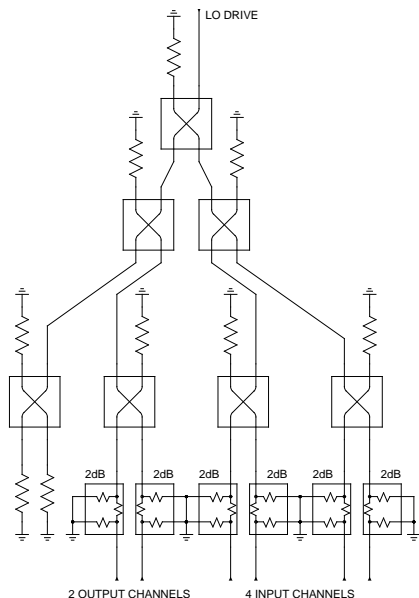

- 75  $\mu$ s output pulse (full scale);
- Isolation is around 77 dB;
- Connect the output to one of the inputs, still 74 dB;
- 8-way splitter: 3 stages of 90° hybrids;



# Outline


## 1 Introduction

## 2 Measurements and Surprises

- Single Tone ADC Characterization
- Spurs
- Amplifier Phase Noise
- Input Channel Coupling
- Output to Input Coupling
- Reflections




# Tricky Power Splitters

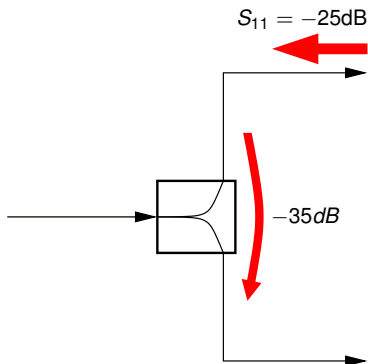

- Power splitters are extremely common in LLRF;
- Datasheets will quote 20–40 dB isolation between output ports;
- That spec assumes that the input port is perfectly matched;
- Due to the sum port mismatch the isolation is 41 dB instead of 60 dB.



# Tricky Power Splitters

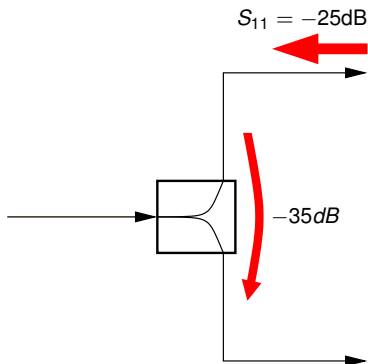


- Power splitters are extremely common in LLRF;
- Datasheets will quote 20–40 dB isolation between output ports;
- That spec assumes that the input port is perfectly matched;
- Due to the sum port mismatch the isolation is 41 dB instead of 60 dB.






# Tricky Power Splitters

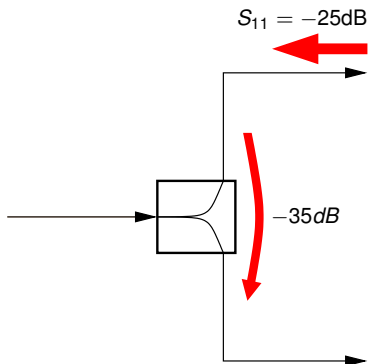

- Power splitters are extremely common in LLRF;
- Datasheets will quote 20–40 dB isolation between output ports;
- That spec assumes that the input port is perfectly matched;
- Due to the sum port mismatch the isolation is 41 dB instead of 60 dB.




# Tricky Power Splitters

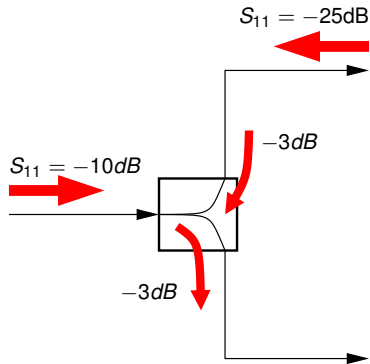

- Power splitters are extremely common in LLRF;
- Datasheets will quote 20–40 dB isolation between output ports;
- That spec assumes that the input port is perfectly matched;
- Due to the sum port mismatch the isolation is 41 dB instead of 60 dB.



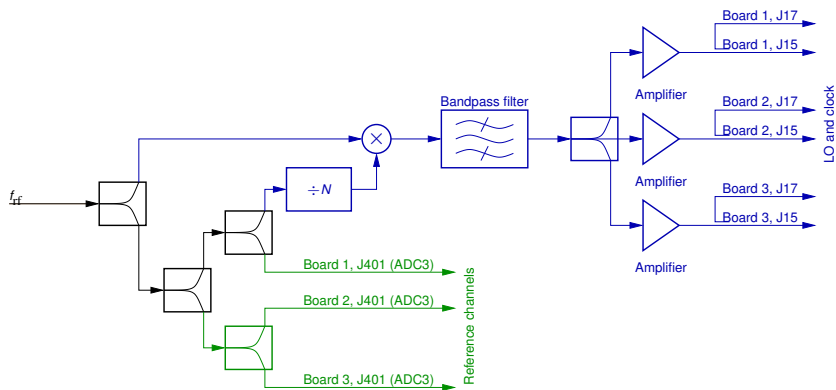
# Real Life Example: Divide and Mix LO Generation



- Reflections in the splitter network change depending on the source impedance;
- Changes in reference level lead to changes in mixer RF and LO port matching.




# Stabilizing Mixer Match

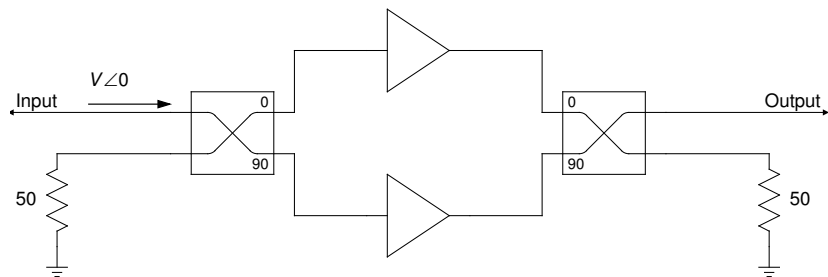

- Inspired by the idea of balanced amplifier matching;
- Drive two identical devices in quadrature;
- Combine outputs appropriately;
- If  $\Gamma_1 = \Gamma_2$ , reflection vanishes;
- In practice, expect 17–20 dB return loss;




# Stabilizing Mixer Match

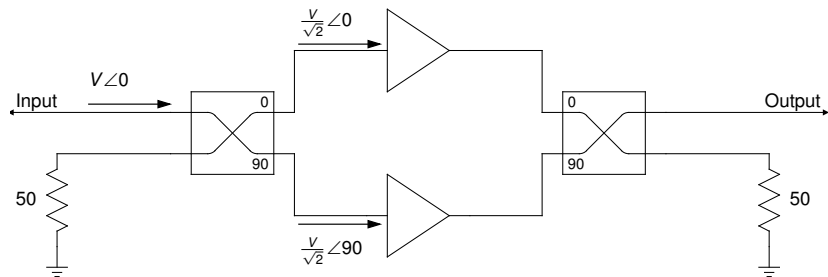

- Inspired by the idea of balanced amplifier matching;
- Drive two identical devices in quadrature;
- Combine outputs appropriately;
- If  $\Gamma_1 = \Gamma_2$ , reflection vanishes;
- In practice, expect 17–20 dB return loss;




# Stabilizing Mixer Match

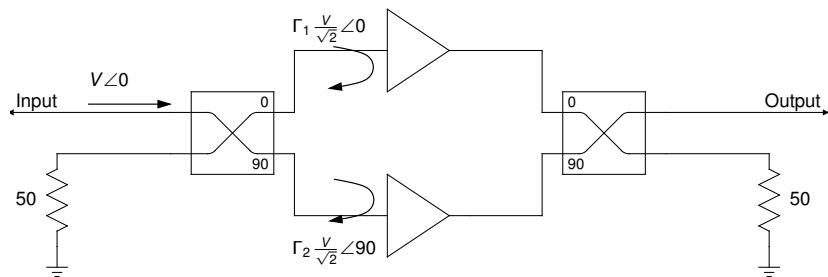

- Inspired by the idea of balanced amplifier matching;
- Drive two identical devices in quadrature;
- Combine outputs appropriately;
- If  $\Gamma_1 = \Gamma_2$ , reflection vanishes;
- In practice, expect 17–20 dB return loss;




# Stabilizing Mixer Match

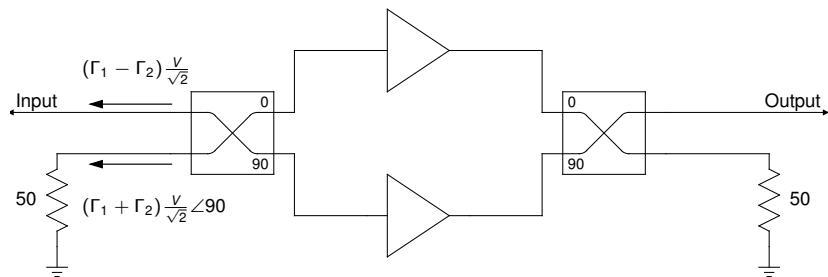

- Inspired by the idea of balanced amplifier matching;
- Drive two identical devices in quadrature;
- Combine outputs appropriately;
- If  $\Gamma_1 = \Gamma_2$ , reflection vanishes;
- In practice, expect 17–20 dB return loss;



# Stabilizing Mixer Match

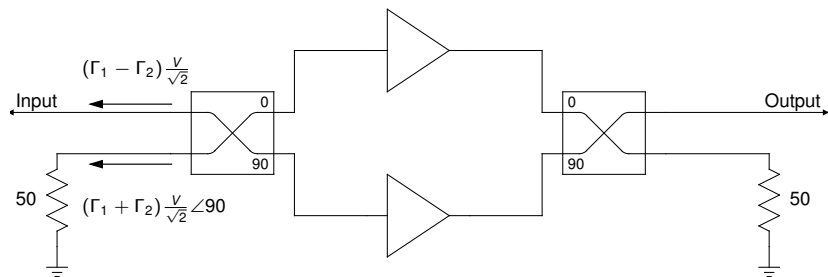


- Inspired by the idea of balanced amplifier matching;
- Drive two identical devices in quadrature;
- Combine outputs appropriately;
- If  $\Gamma_1 = \Gamma_2$ , reflection vanishes;
- In practice, expect 17–20 dB return loss;





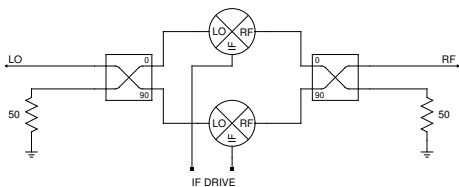
# Stabilizing Mixer Match: Termination Insensitive Mixer



- Two options for IF drive: common mode or differential;
- Differential also reduces LO-to-RF coupling by 20 dB;
- Reflection coefficient on LO and RF ports is around 0.1 and shows very little change with incident power;
- Turns out this design is called Termination Insensitive Mixer;
- A figure from MITEQ Application Note on TIMs.



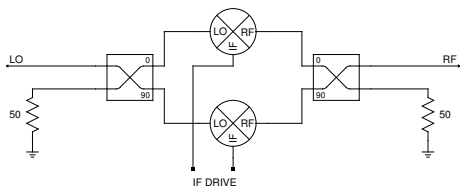
# Stabilizing Mixer Match: Termination Insensitive Mixer



- Two options for IF drive: common mode or differential;
- Differential also reduces LO-to-RF coupling by 20 dB;
- Reflection coefficient on LO and RF ports is around 0.1 and shows very little change with incident power;
- Turns out this design is called Termination Insensitive Mixer;
- A figure from MITEQ Application Note on TIMs.



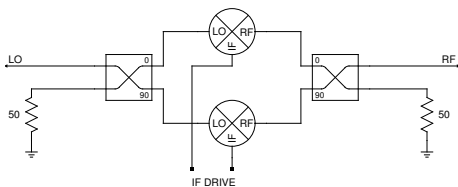
# Stabilizing Mixer Match: Termination Insensitive Mixer



- Two options for IF drive: common mode or differential;
- Differential also reduces LO-to-RF coupling by 20 dB;
- Reflection coefficient on LO and RF ports is around 0.1 and shows very little change with incident power;
- Turns out this design is called Termination Insensitive Mixer;
- A figure from MITEQ Application Note on TIMs.


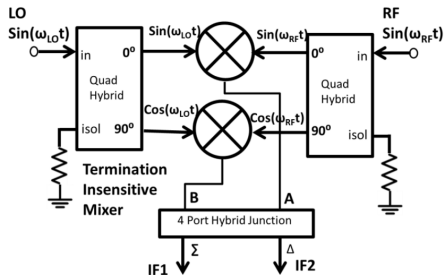
# Stabilizing Mixer Match: Termination Insensitive Mixer



- Two options for IF drive: common mode or differential;
- Differential also reduces LO-to-RF coupling by 20 dB;
- Reflection coefficient on LO and RF ports is around 0.1 and shows very little change with incident power;
- Turns out this design is called Termination Insensitive Mixer;
- A figure from MITEQ Application Note on TIMs.



# Summary

- Most important task of the LLRF receiver is keeping out all signals, but one;
- Never trust the datasheets or, possibly, your understanding of them — I've spent years misreading and misusing the specs;
- Keep it simple;
- When in doubt - prototype!



# Summary

- Most important task of the LLRF receiver is keeping out all signals, but one;
- Never trust the datasheets or, possibly, your understanding of them — I've spent years misreading and misusing the specs;
- Keep it simple;
- When in doubt - prototype!



# Summary

- Most important task of the LLRF receiver is keeping out all signals, but one;
- Never trust the datasheets or, possibly, your understanding of them — I've spent years misreading and misusing the specs;
- Keep it simple;
- When in doubt - prototype!



# Summary

- Most important task of the LLRF receiver is keeping out all signals, but one;
- Never trust the datasheets or, possibly, your understanding of them — I've spent years misreading and misusing the specs;
- Keep it simple;
- When in doubt - prototype!





# Acknowledgments

- I'd like to thank many people for listening patiently to my (LL)RF rants and for offering advice.
- I would especially like to thank Dan Van Winkle and Larry Doolittle for many enlightening discussions.

